

KATHMANDU UNIVERSITY
End Semester Examination [C]
January, 2018

Marks scored:

Level : B.Sc.
Year : II

Course : EEG 202
Semester: I

Exam Roll No. :

Time: 30 mins

F. M. : 20

Registration No.:

Date JAN 12 2018

SECTION "A"
[20 × 1=20 marks]


Choose the most appropriate option. **Symbols** have their usual meaning.

1. The NOR gate output will be high if the two inputs are _____
a. 00 b. 01 c. 10 d. 11
2. Which of the following expression is correct for the given K-Map?

AB\CD	00	01	11	10
00	0	0	0	1
01	0	0	0	1
11	0	0	0	1
10	1	0	0	1

- a. $\bar{B} \bar{C} + \bar{B} \bar{D}$ b. $A \bar{C} + \bar{B} \bar{D}$ c. $C \bar{D} + A \bar{B} \bar{C}$ d. $C \bar{D} + A \bar{B} \bar{D}$
3. The number of control lines for a 16 – to – 1 multiplexer is _____
a. 2 b. 3 c. 4 d. 5
4. How many flip-flops are required for mod-12 counter?
a. 6 b. 5 c. 4 d. 3
5. The binary equivalent of gray code 10011 is _____
a. 11100 b. 11001 c. 10001 d. 11101
6. The simplified expression for the following expression, $Y = AB+AC+BD+CD$ is given by
a. $(A+D)(B+C)$ b. $(A.D)(B+C)$ c. $(A+\bar{D})(B.C)$ d. $(A+D)(B.C)$
7. The digital logic family which has minimum power dissipation is _____
a. TTL b. RTL c. DTL d. CMOS
8. Which of the following is universal gate?
a. X-OR b. X- NOR c. OR d. NOR
9. A combinational circuit which converts binary information from n input lines to a maximum of 2^n unique output lines is known as _____
a. Encoder b. Decoder c. Multiplexer d. Demultiplexer
10. The device which changes data from parallel to serial is known as _____
a. Encoder b. Decoder c. Multiplexer d. Demultiplexer
11. A 4 bit counter counts up to _____
a. 4 b. 3 c. 15 d. 16

 12. Which of the following expression represents the DeMorgan's law?
 a. $\overline{A+B} = \overline{A} + \overline{B}$ b. $\overline{A+B} = A+B$ c. $\overline{A+B} = A.B$ d. $\overline{A+B} = \overline{A}. \overline{B}$
13. Which of the following Hexadecimal number corresponds to the binary number 10110001101011.11110010?
 a. $(C6B.E2)_{16}$ b. $(3C6B.F2)_{16}$ c. $(2C5B.E2)_{16}$ d. $(2C6B.F2)_{16}$
14. For JK flip flop with $J=0, K=1$, the output after clock pulse will be _____
 a. Low b. High c. No change d. Invalid
15. The excess-3 code of decimal 9 is represented by
 a. 1001 b. 1011 c. 0101 d. 1100
16. The state transition diagram corresponds to the _____ flip-flop.



- a. SR flip-flop b. JK flip-flop c. D flip-flop d. T flip-flop
17. Which of the following gate can be used to construct a SR latch?
 a. X-OR b. X-NOR c. NOT d. NOR
18. The characteristic equation for the JK flip flop is given by
 a. $Q(\text{next}) = JQ' + K'Q$ b. $Q(\text{next}) = JQ + K'Q$
 c. $Q(\text{next}) = JQ' + KQ$ d. $Q(\text{next}) = J'Q' + K'Q$
19. A 5 bit parallel input serial output shift register requires _____
 a. 5 SR flip flops b. 5 JK flip flops c. 5 D flip flops d. 5 T flip flops
20. Internal logic of ROM includes _____
 a. Array of AND gates b. Array of OR gates
 c. AND gates and a decoder d. OR gates and a decoder

KATHMANDU UNIVERSITY
End Semester Examination [C]
January, 2018

JAN 12 2018

Level : B.Sc.
Year : II
Time : 2 hrs. 30 mins.

Course : EEG 202
Semester: I
F. M. : 55

SECTION "B"
[5 Q. × 11 = 55 marks]

Attempt *ANY FIVE* questions. Figure in the margin indicates the full mark. Students are required to answer in their own words as far as practicable. Symbols have their usual meanings.

1.
 - a) Define radix, binary logic and Boolean algebra. How is binary logic different than arithmetic logic? [2]
 - b) Which gates are called as the universal gates? What are its advantages? [2]
 - c) Explain the design procedure for combinational circuit. [2]
 - d) What is the function of enable input in a multiplexer? Construct a logic circuit for 4 to 1 multiplexer. [1+4]
2.
 - a) What are called don't care conditions? Simplify the following Boolean function using K-map
 $F(w,x,y,z) = \sum(1,3,7,11,15)$ which has the don't care conditions
 $d(w,x,y,z) = \sum(0,2,5)$ [1+3]
 - b) Design logic circuit for BCD adder by using 4 bit binary adders. [5]
 - c) Why is it necessary to use tabulation method for simplifying Boolean expressions instead of K-map? Justify your answer. [2]
3.
 - a) Why is carry lookahead generator important? Draw logic circuit for carry lookahead generator with the help of generalized expression for carry propagation. [2+4]
 - b) Design a three bit synchronous counter and explain the operation with the help of time diagram. [5]
4.
 - a) Why is code conversion important? Draw the K-maps for BCD to excess-3 code converter and construct the logic diagram for BCD to excess-3 code converter. [1+4]
 - b) Construct a 5 to 32 line decoder with four 3 to 8 line decodes with enable and 2 to 4 line decoder. Use block diagram for components. [3]
 - c) Implement the following Boolean functions using PLA
 $F_1(A,B,C) = \sum(0,1,2,4)$ and $F_2(A,B,C) = \sum(0,5,6,7)$ [3]
5.
 - a) Draw the characteristic table and excitation table for JK flip-flop and convert the JK flip-flop into T flip-flop with the help of excitation table. How does JK flip-flop avoid the race condition observed in SR flip-flop? [6]
 - b) Write the applications of shift registers. Draw logic circuit for bidirectional shift registers and also explain the operation in detail. [1+4]

6.

- a) Why asynchronous counters are also known as ripple counter? Differentiate between synchronous and asynchronous counter and design a logic circuit for three bit asynchronous up/down counter. [5]
- b) Derive the state table and the state diagram for the following sequential circuit as shown in figure (a) where x , y represent the input, output respectively and A , B represent states of the flip-flops. [6]

 


Figure (a)